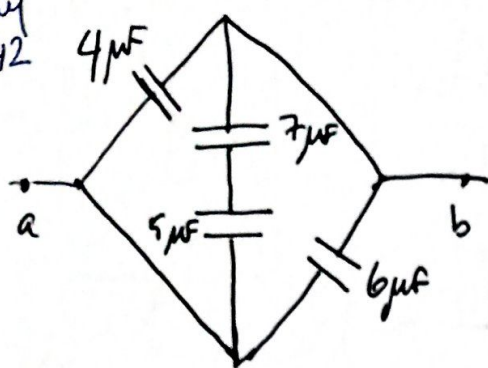


Serway
16.42



a) what's $C_{eq} = ?$

b) circuit is powered by V_{ab} potential.




if charge at $4 \mu F$ Q_1

$7 \mu F$ Q_2


$5 \mu F$ Q_3

$6 \mu F$ Q_4

find the relations between charges?

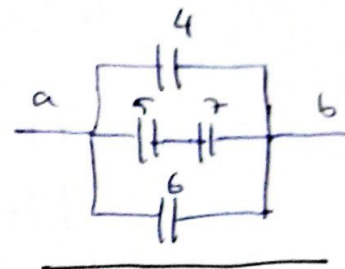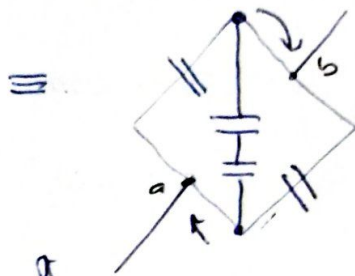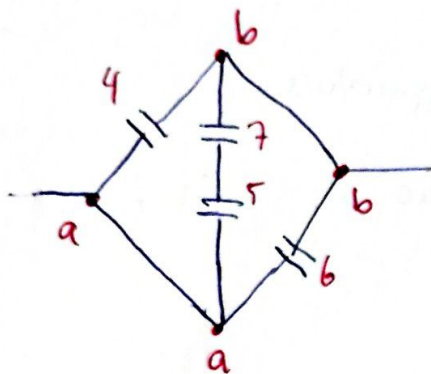

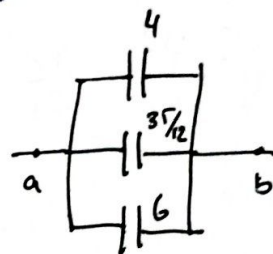
$$5 - 7 \mu F \text{ series} \Rightarrow \left(\frac{1}{5} + \frac{1}{7} \right)^{-1} = \frac{35}{12} \mu F$$



} parallel
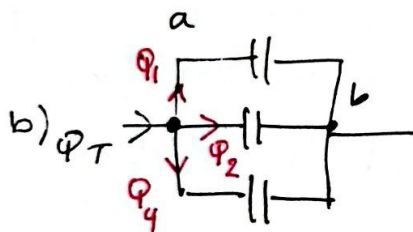
$$C_{eq} = 4 + 6 + \frac{35}{12} = \frac{155}{12} \mu F$$




$Q_3 = Q_2$ since series

$$V_{ab} = \frac{Q_1}{4} = \frac{Q_2}{35/12} = \frac{Q_4}{6}$$

$$\text{if } Q_1 = Q \quad Q_4 = \frac{6}{4} Q = \frac{3}{2} Q$$

$$Q_2 = Q_3 = \frac{35}{48} Q$$

16.37 Serway

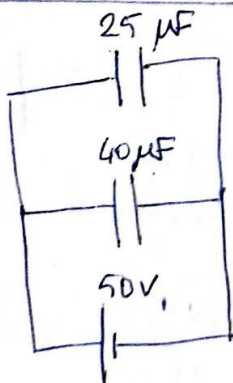

capacitors are charged with 50V.

the battery is disconnected; and the the capacitors are separated;

if capacitors are connected oppositely

→ what are their final charges?

what " " " potential.

$$\frac{Q}{C} = V$$



$$Q_1 = (50) 25 \mu F V = 1250 \mu C$$

$$Q_2 = 50 (40) \mu F V = 2000 \mu C$$



$$V_{ab} = 50V$$

$$V_{ab}' = ?$$

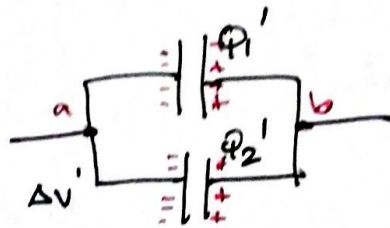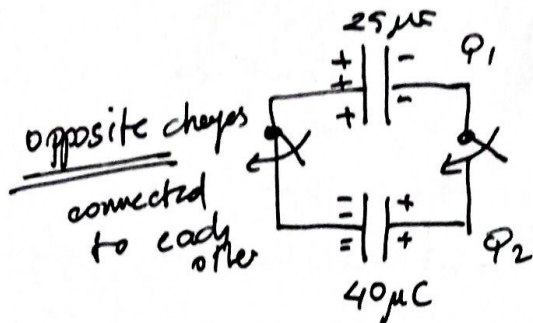

Q total will be shared between capacitors.

$$Q_T = Q_1 - Q_2 = 1250 - 2000 = -750 \mu C$$

$$|Q_T| = 750 \mu C = Q_1' + Q_2'$$

$$\Delta V' = \frac{Q_1'}{C_1} = \frac{Q_2'}{C_2} \Rightarrow \frac{Q_1'}{25} = \frac{Q_2'}{40} \quad Q_1' = \frac{25}{40} Q_2' = \frac{5}{8} Q_2'$$

$$Q_1' + Q_2' = 750 = Q_T$$

$$\frac{5}{8} Q_2' + Q_2' = \frac{13 Q_2'}{8} = 750$$

$$\left\{ \begin{array}{l} Q_2' = 461.5 \mu C \\ Q_1' = 288.5 \mu C \end{array} \right.$$

summary

$$V_0 = 50V;$$

$$V' = 11.5V$$

$$\left\{ \begin{array}{l} \Delta V' = \frac{Q_1'}{C_1} = \frac{Q_2'}{C_2} \\ \Delta V' = \frac{288.5}{25} = 11.5V \\ \text{or } \frac{461.5}{40} = 11.5V \end{array} \right.$$

\Rightarrow ratio of energy stored before & after?

$$U_T = U_1 + U_2 = \frac{1}{2} C_1 \Delta V^2 + \frac{1}{2} C_2 \Delta V^2 = \frac{1}{2} (25 + 40) 50^2 = 81250 \mu J$$

$$U_T' = U_1' + U_2' = \frac{1}{2} C_1 \Delta V'^2 + \frac{1}{2} C_2 \Delta V'^2 = \frac{1}{2} (25 + 40) 11.5^2 = 4298 \mu J$$


$$\text{Lost energy} = 81250 - 4298 = 76952 \mu J = |\Delta U| = |U_T' - U_T|$$

$$\text{percent of lost energy to initial} = \frac{\Delta U}{U_T} = 0.95 \Rightarrow 95\% \text{ lost}$$

$$\Delta U = \frac{1}{2} (C_1 + C_2) (\Delta V'^2 - \Delta V^2)$$









$$= \frac{1}{2} (C_1 + C_2) \Delta V^2 \left[\frac{11.5^2 - 50^2}{50^2} \right] = 0.947 = 94.7\%$$

(24.63)

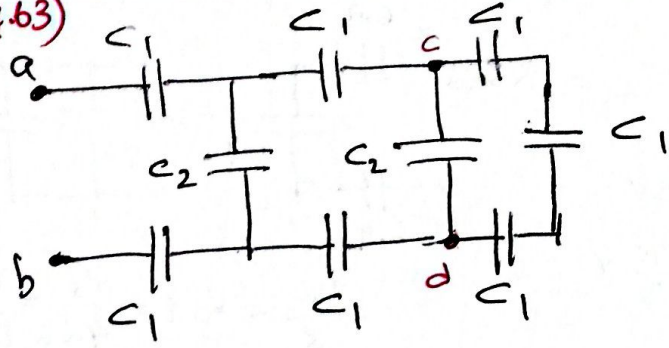


$C_1 = 6.9 \mu F$
 $C_2 = 4.6 \mu F$
 $V_{ab} = 420 V$

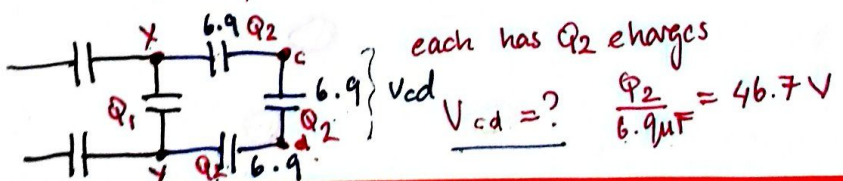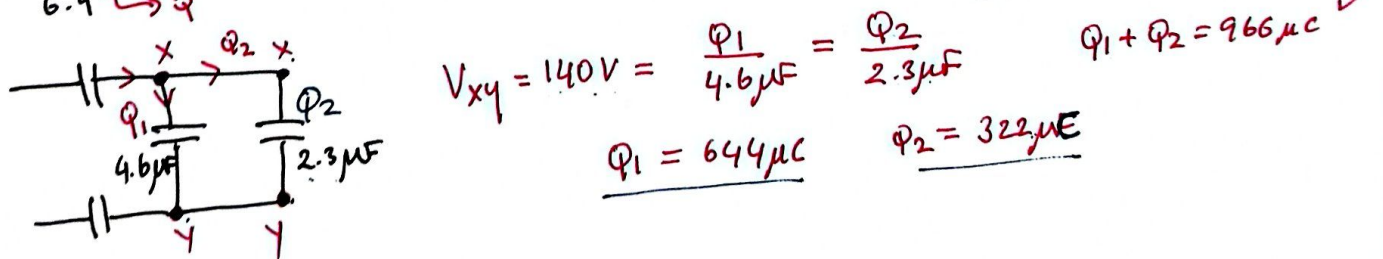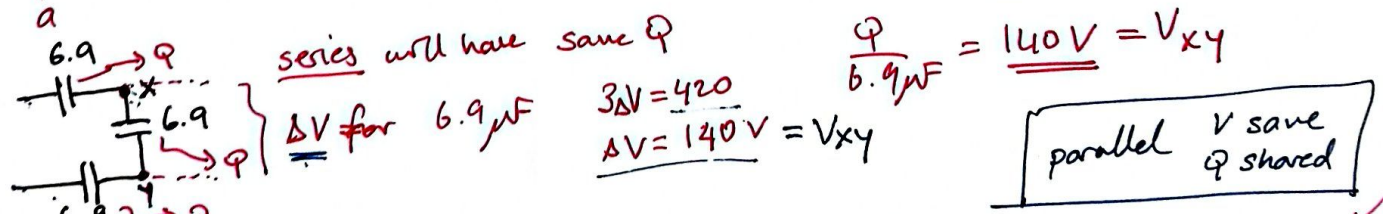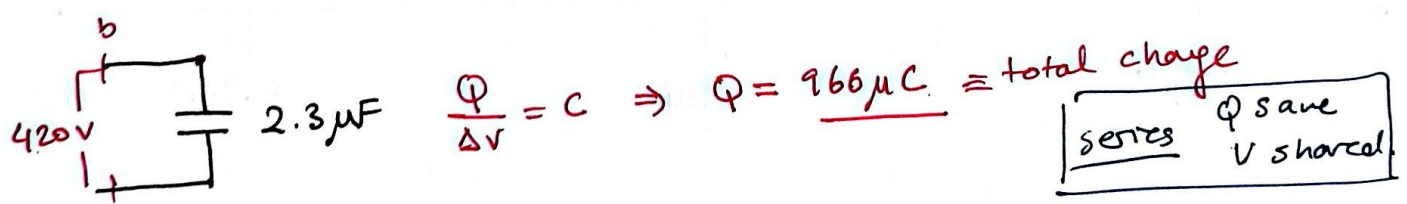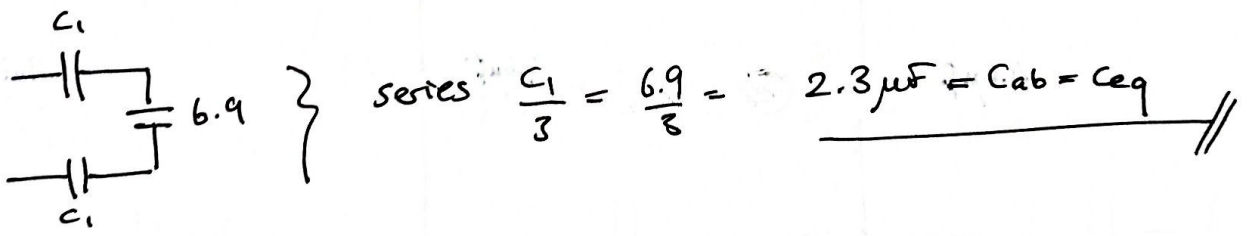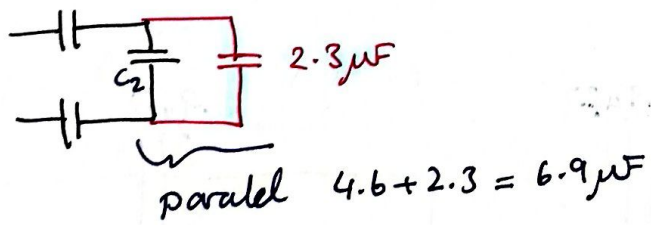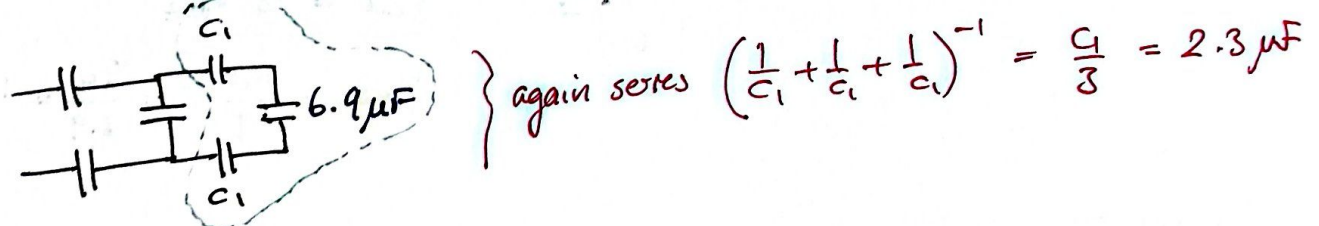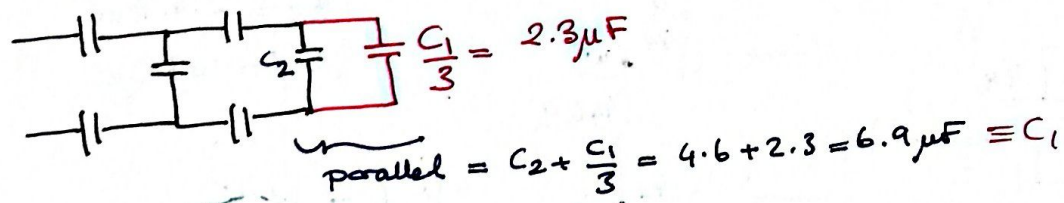- a) $C_{eq} = ?$ $C_{ab} = ?$
- b) charge distribution? charge on each?
- c) $V_{cd} = ?$




(24.63)

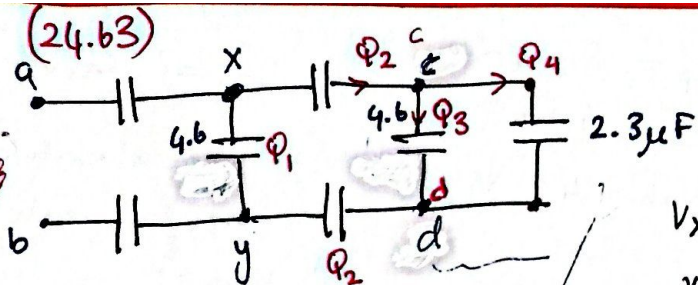

$$V_{xy} = 3V_{cd}$$

$$V_{xy} = 140V$$

$$V_{cd} = \frac{140}{3} V$$

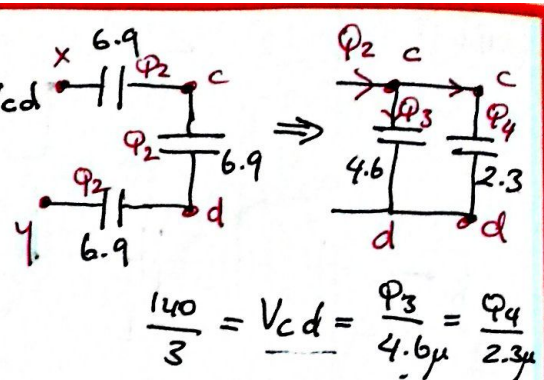


$$\frac{140}{3} = V_{cd} = \frac{Q_3}{4.6 \mu} = \frac{Q_4}{2.3 \mu}$$

$$Q_3 = 214.7 \mu C$$

$$Q_4 = 107.3 \mu C$$

Lastly

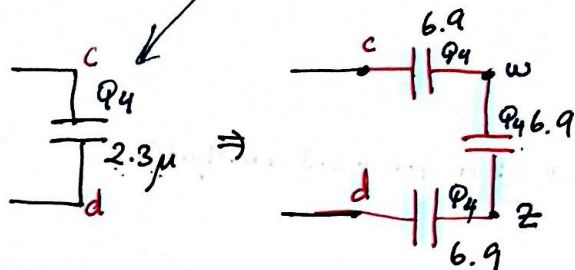


$$V_{cd} = 3V_{wz}$$

$$V_{wz} = \frac{140}{9} V = \frac{Q_4}{6.9} = 15.56 V$$

Summary

$$V_{ab} = 420V$$

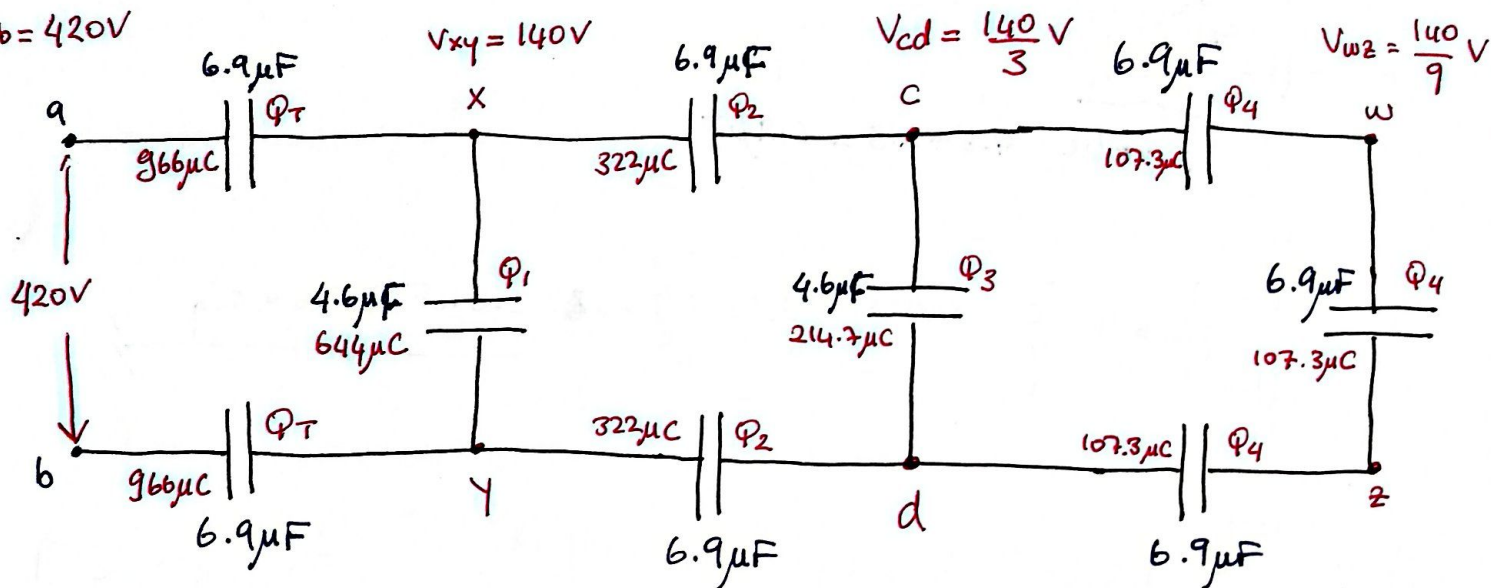

$$V_{ab} = 420V$$

$$V_{xy} = 140V$$

$$V_{cd} = \frac{140}{3} V$$

$$V_{wz} = \frac{140}{9} V$$

$$Q_T = 966 \mu C$$

$$Q_1 = 644 \mu C$$

$$Q_2 = 322 \mu C$$


$$Q_3 = 214.7 \mu C$$

$$Q_4 = 107.3 \mu C$$

$$C_{eq} = 2.3 \mu F$$

24.27) A parallel plate with area A ; separation x has $+Q, -Q$ charges on its plates. The capacitor is disconnected from battery & charges are fixed.

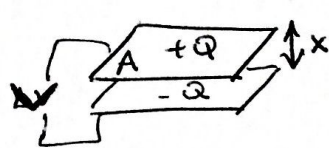
a) what's the total energy stored in the capacitor?



$$C = \epsilon_0 \frac{A}{x} \quad U = \frac{Q^2}{2C} = \frac{QV}{2} = \frac{1}{2} CV^2$$

$$U = \frac{Q^2}{2\epsilon_0 \frac{A}{x}} = \frac{Q^2 x}{2\epsilon_0 A} = \frac{QV}{2}$$

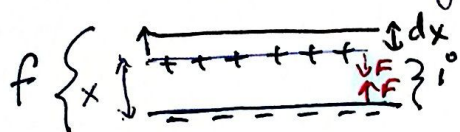b) The plates are pulled apart an additional ~~force~~ ^{displacement} dx . What's the change in the stored energy? $\Delta U = ?$



$$U_i \rightarrow U_f$$

$$\frac{Q^2 x}{2\epsilon_0 A} \rightarrow \frac{Q^2 (x+dx)}{2\epsilon_0 A}$$

$$\Delta U = U_f - U_i$$


$$= \frac{Q^2 dx}{2\epsilon_0 A} = dU$$

c) The plates are attracting each other with force F , what's F ?

$$W = \vec{F} \cdot d\vec{x} < 0$$

$$W = -\Delta U \text{ (phys I)}$$

$$-F dx = -dU$$

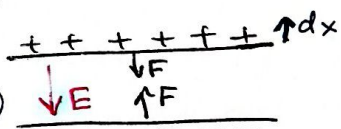

$dW = F dx$ amount of work for F to move dx .

$dW = dU$ work done = change in pot. energy

$$dW = F dx = dU \quad F = \frac{dU}{dx} = \frac{Q^2 dx / 2\epsilon_0 A}{dx}$$

remember:


for metal surface $E = \frac{\sigma}{\epsilon_0} = \frac{Q/A}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$

$$\frac{Q^2}{2\epsilon_0 A} = F \neq QE = \frac{Q^2}{\epsilon_0 A}$$

$$* F = \frac{Q^2}{2\epsilon_0 A} \text{ (Force between capacitor plates)}$$

$$\{ F = QE = \frac{Q^2}{\epsilon_0 A}$$

$$F \neq QE; F = \frac{QE}{2}$$

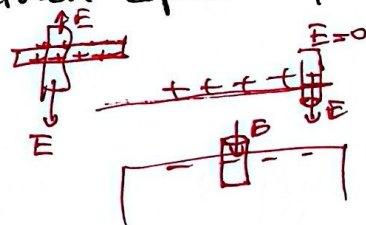

24.37 Two parallel plates have equal opposite charges. In vacuum E is $E = 3.2 \times 10^5 \frac{V}{m}$; when the space between plates is filled with a dielectric κ $E' = 2.5 \times 10^5 \frac{V}{m}$ (with κ). a) what's σ_i (induced) charge density on the dielectric surface. b) what's κ ?

$$+Q \text{ --- } \downarrow E = 3.2 \times 10^5 \frac{V}{m}$$

$$+Q \text{ --- } \downarrow E' = 2.5 \times 10^5 \frac{V}{m}$$

$$E' = \frac{E}{\kappa} \Rightarrow \kappa = \frac{3.2 \times 10^5}{2.5 \times 10^5} = 1.28 = \kappa$$

$$E = \frac{\sigma}{\epsilon_0}$$

$$E' = \frac{\sigma'}{\epsilon_0} = \frac{\sigma - \sigma_i}{\epsilon_0} = \frac{\sigma}{\epsilon_0 \kappa} \Rightarrow \sigma_i = \sigma \left(1 - \frac{1}{\kappa}\right)$$

$$\sigma_i = \sigma \left(1 - \frac{1}{\kappa}\right) = E \epsilon_0 \left(1 - \frac{1}{1.28}\right)$$

$$\text{also } \sigma = \epsilon_0 E = 28.3 \times 10^{-7} \text{ C/m}^2$$

$$\sigma = 2830 \text{ nC/m}^2$$


$$\sigma' = \frac{\sigma}{\kappa} = 2213 \text{ nC/m}^2$$

$$\sigma_i = 3.2 \times 10^5 \times 8.85 \times 10^{-12} \left(\frac{0.28}{1.28}\right)$$

$$\sigma_i \approx 6.2 \times 10^{-7} \text{ C/m}^2$$

$$\sigma_i = 620 \times 10^{-9} \text{ C} = 620 \text{ nC/m}^2$$

explanation

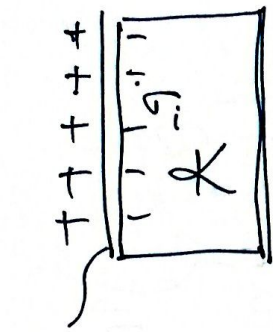

$$E = \frac{\sigma}{\epsilon_0}$$

$$E' = \frac{\sigma'}{\epsilon_0} = \frac{\sigma - \sigma_i}{\epsilon_0}$$

$$3.2 \times 10^{+5}$$

$$8.85 \times 10^{-12}$$

$$E' = \frac{\sigma - \sigma_i}{\epsilon_0}$$

$$\sigma' = \sigma - \sigma_i$$

$$\frac{K=1 \text{ vacuum}}{E}$$

$$V$$

$$\sigma$$

$$\left(2.5 \times 10^5 \times 8.85 \times 10^{-12} \right) \quad \sigma - \sigma_i$$

$$E' = \frac{E}{K}$$

$$V' = \frac{V}{K}$$

$$\sigma' = \frac{\sigma}{K} = \left[\frac{\sigma - \sigma_i}{K} \right]$$

$$\sigma_i = \sigma - \frac{\sigma}{K} = \sigma \left(1 - \frac{1}{K} \right)$$


$$\underline{K=2}$$

$$\sigma_i = \sigma \left(\frac{2-1}{2} \right) = \frac{\sigma}{2}$$

$$\sigma_i = \sigma \left(\frac{K-1}{K} \right)$$

K ~ capacity to be able to charge on its surface

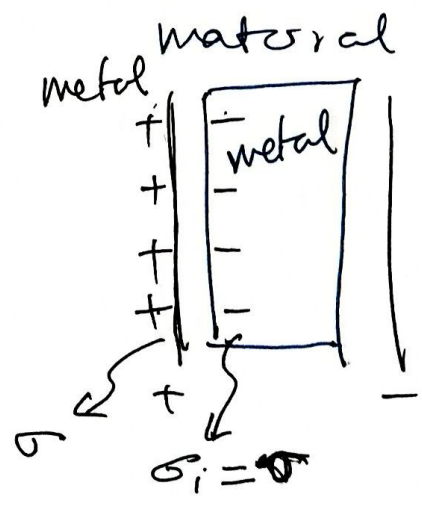half of the initial charge is induced on the ~~plate~~ dielectric material



$$\sigma_i < \sigma$$

$$\underline{K > 1}$$